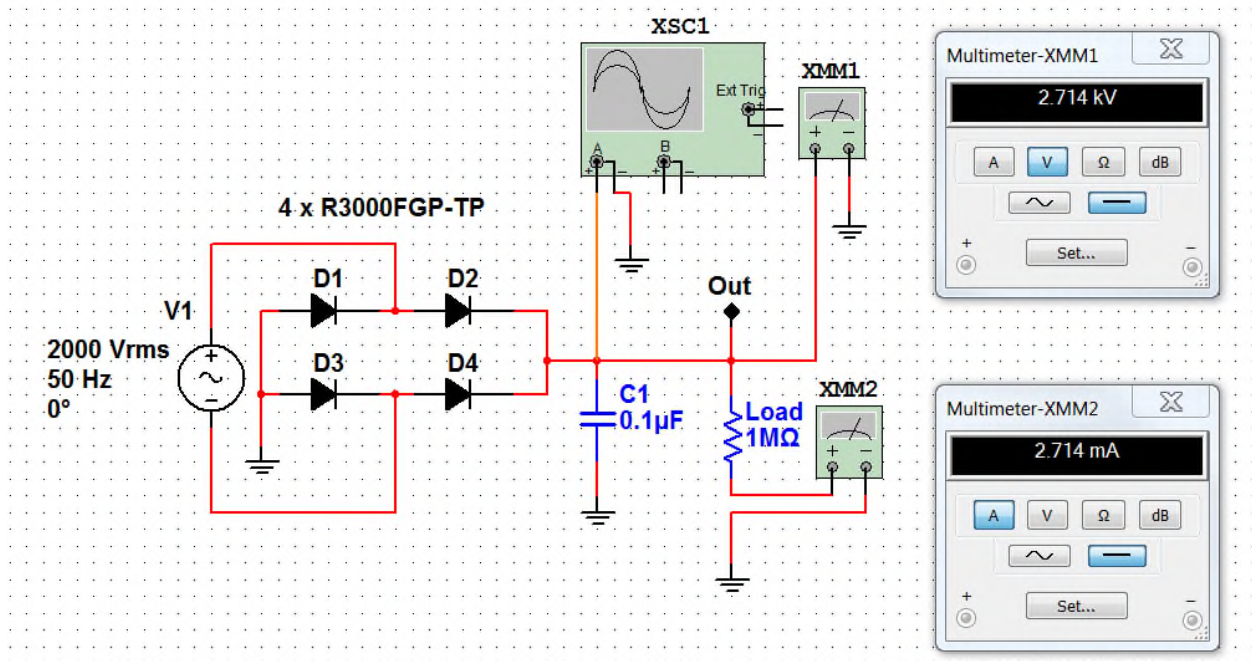



The following simulations was done with National Instruments Ni Multisim 11.0

With the circuit below that have a transformer that has an output of 2000 Volt RMS we will get a DC (average) output of 2714 Volts with a load of 1 Mega Ohm. The load current will be 2.714 mA.




The diodes used are R3000FGP-TP from Digikey, part number R3000FGP-TPMSCT-ND. Price 0.87 US \$.

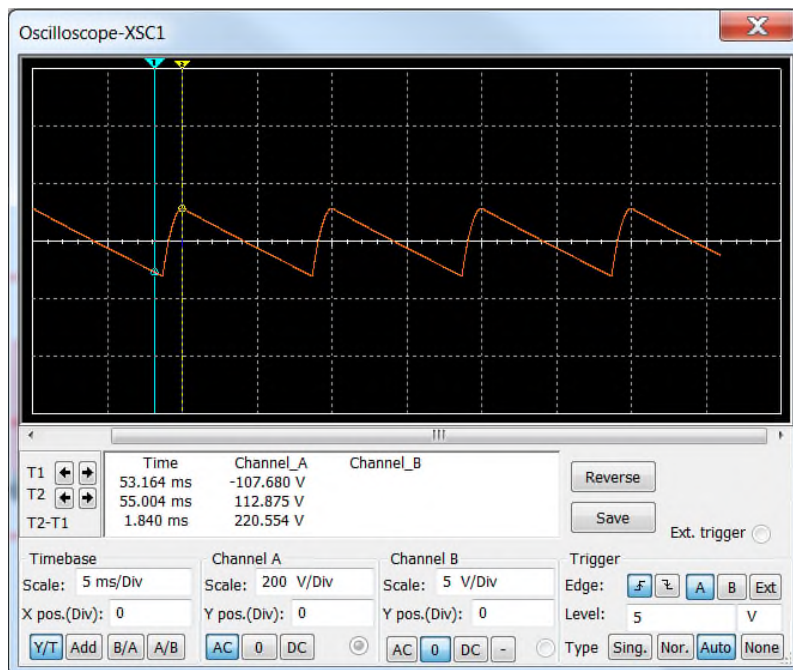The ripple will be as below; the ripple will be about 234 V peak to peak.



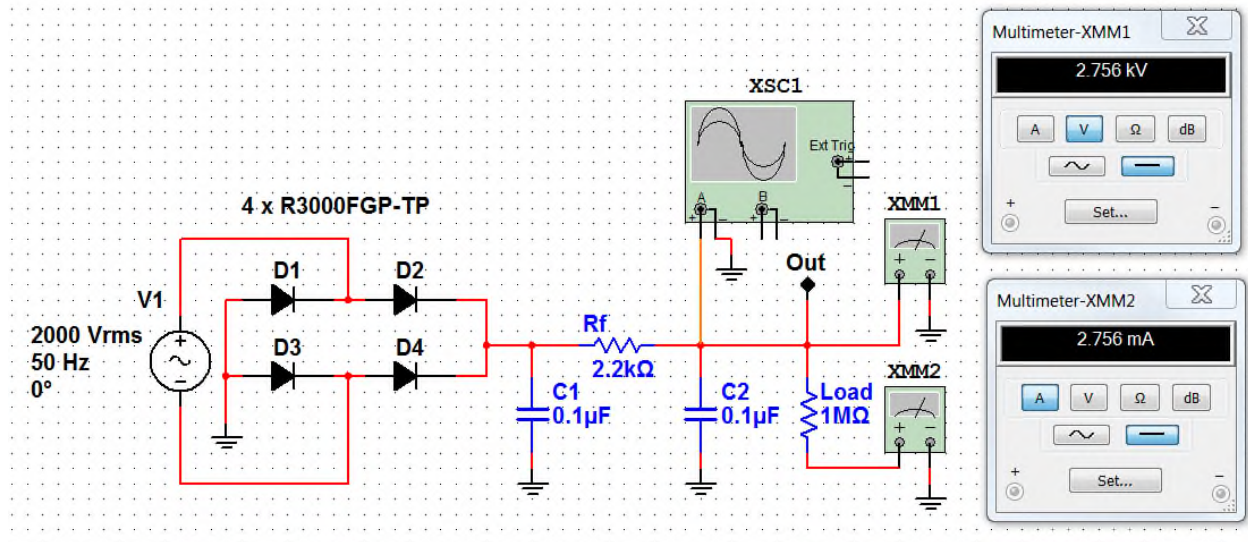
An alternative solution would be the circuit below. In this case we use both the 0.1 uF capacitors and have added a 2.2 KOhm resistor between them:



In this case the ripple will be about 120 Volt peak to peak as can be see below:



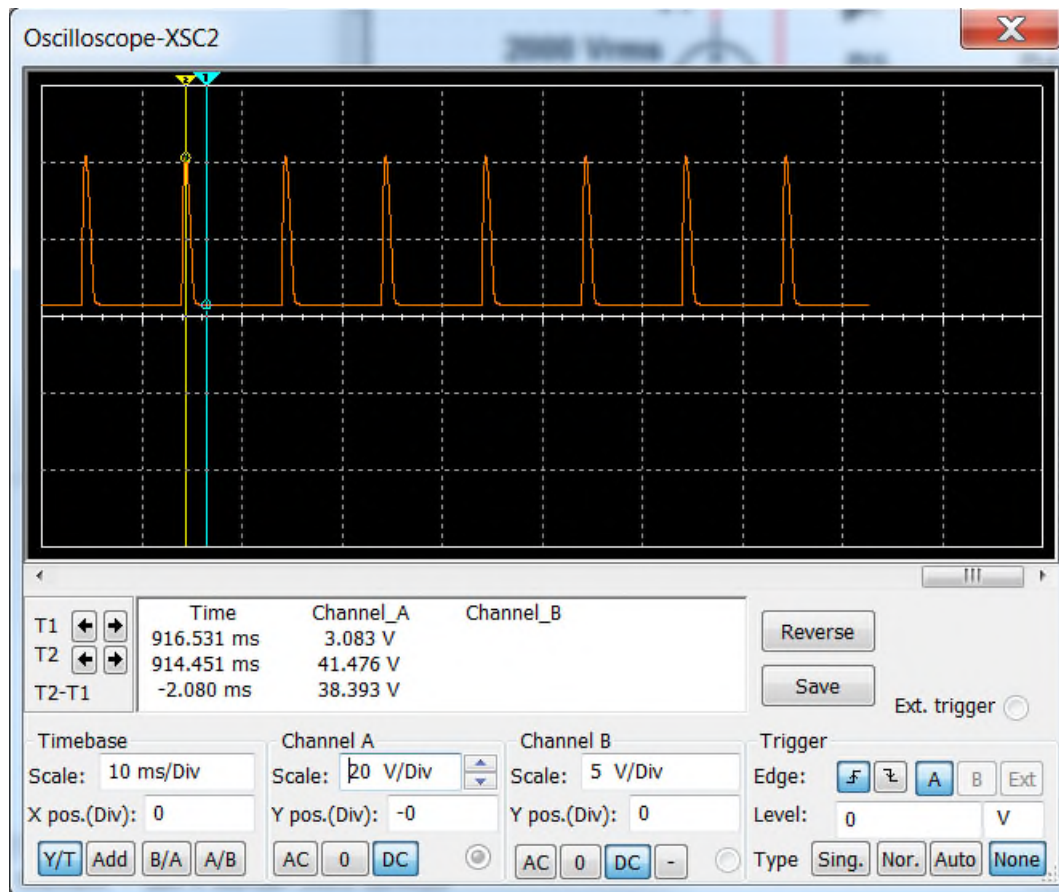The voltage drop over Rf will look like below and is in the order of 40 Volt.



In any case the filtering of the circuit(s) will be pretty bad. Best case gives $120 / 2756 \sim 4.4 \%$

A better solution would be to use a High Voltage, low noise, DC/DC converter as can be found in by this link: <https://www.analog.com/media/en/technical-documentation/application-notes/an118fb.pdf>

Regards

/Bo, SM6FIE